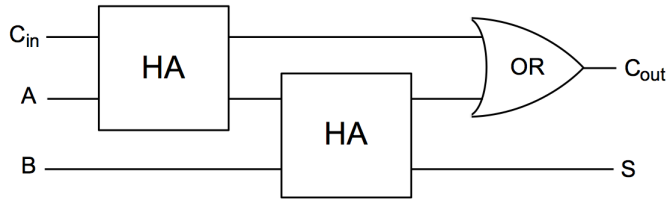


# Assignment 14

Due by class time Tuesday, November 8


1. A logic diagram and truth table for a Full-Adder circuit (*FA*) is given below:



C <sub>in</sub>	A	B	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


- (a) Find the corresponding matrix for *FA*.
- (b) Write an equivalent expression for *FA* that combines the matrices *HA*, *IDEN*, and *OR* using matrix multiplication and the tensor product (where *HA* is the matrix for the Half-Adder circuit from the previous assignment, and *IDEN* is the  $2 \times 2$  identity matrix).

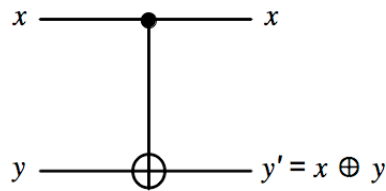2. The symbol for the controlled-NOT gate (CNOT) and its truth table are shown below, with the output  $y' = x \oplus y$ :




x	y	x	y'
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

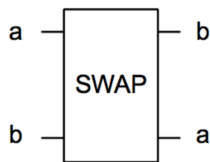- (a) Show how to construct a COPY gate from a single CNOT gate.
- (b) A SWAP gate takes two input bits and simply swaps their order, as shown in the diagram and truth table below. Show how to construct a SWAP gate from three CNOT gates. Hint: the XOR identities  $z \oplus z = 0$  and  $z \oplus 0 = z$  may be useful.



a	b	b	a
0	0	0	0
0	1	1	0
1	0	0	1
1	1	1	1

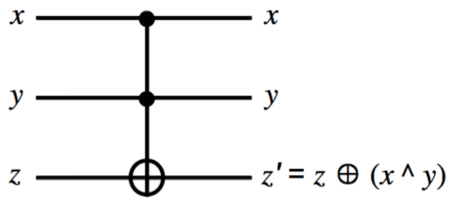3. The symbol for a Toffoli gate and its corresponding truth table are shown below, where the output  $z' = z \oplus (x \wedge y)$ :



x	y	z		x	y	z'
0	0	0		0	0	0
0	0	1		0	0	1
0	1	0		0	1	0
0	1	1		0	1	1
1	0	0		1	0	0
1	0	1		1	0	1
1	1	0		1	1	1
1	1	1		1	1	0

- (a) Show how to construct a NAND gate using a single Toffoli gate.
- (b) Show how to construct a NOR gate using three Toffoli gates.
- (c) Show how to construct an OR gate using three Toffoli gates.
- (d) Show how to construct an OR gate using only two Toffoli gates.